



# EE 618

# Microelectronics Lab

---

TA: Kailash Prasad  
PhD in Electrical Engineering

Instructor: Prof. Joycee Mekie



# Outline

---

- **Introductions**
- Verilog Syntax
- Structural Modelling
- Behavioural Modelling
- State Machine
- Random but Important Stuff



---

# Introduction



# The Verilog Language

---

- HDL is a language that describes the hardware of digital systems in a textual form.
- It resembles a programming language, but is specifically oriented to describing hardware structures and behaviors.
- The main difference with the traditional programming languages is HDL's representation of extensive parallel operations whereas traditional ones represents mostly serial operations.
- The most common use of a HDL is to provide an alternative to schematics.
- Most commonly-used languages in digital hardware design (other - VHDL)



# How Verilog Is Used

---

- Virtually every chip (FPGA, ASIC, etc.) is designed in part using one of these two languages
- Behavioral modeling with some structural elements
- “Synthesis subset”
  - Can be translated using Synopsys’ Design Compiler or others into a netlist
- Design written in Verilog
- Simulated to death to check functionality
- Synthesized (netlist generated)
- Static timing analysis to check timing



```
module top_four_bit_comparator(A,B,A_greater,B_greater,Both_equal);
    input [3:0] A,B;
    output A_greater,B_greater,Both_equal;

    wire a,b,c,d,e,f,g,h,i;
    //A_greater cases
    assign a = A[3]&(~B[3]);
    assign b = ~(A[3]^B[3])&(A[2]&(~B[2]));
    assign c = ~(A[3]^B[3])&(A[2]^B[2])&(A[1]&(~B[1]));
    assign d = ~(A[3]^B[3])&(A[2]^B[2])&(A[1]^B[1])&(A[0]&(~B[0]));

    //B_greater Cases

    assign e = B[3]&(~A[3]);
    assign f = ~(B[3]^A[3])&(B[2]&(~A[2]));
    assign g = ~(B[3]^A[3])&(B[2]^A[2])&(B[1]&(~A[1]));
    assign h = ~(B[3]^A[3])&(B[2]^A[2])&(B[1]^A[1])&(B[0]&(~A[0]));

    //equal case
    assign i = ~(B[3]^A[3])&(B[2]^A[2])&(B[1]^A[1])&(B[0]^A[0]);

    assign A_greater = a|b|c|d;
    assign B_greater = e|f|g|h;
    assign Both_equal= i;

endmodule
```



```
module onebitcomp(
    input a1,
    input b1,
    output gt1,
    output eq1,
    output lt1
);
    wire a1bar,b1bar;
    not g1(b1bar,b1);
    not g2(a1bar,a1);
    assign gt1=a1&b1bar;
    assign eq1=~(a1^b1);
    assign lt1= a1bar&b1;
endmodule
```

```
module twobitcomp(
    input [1:0] A,
    input [1:0] B,
    output [2:0] f
);
    wire gt0,eq0,lt0,gt1,eq1,lt1;
    onebitcomp roshni(A[1],B[1],gt1,eq1,lt1);
    onebitcomp req(A[0],B[0],gt0,eq0,lt0);
    assign f=gt1?3'b100:{gt0,eq0,lt0};
endmodule
```

```
module top_FOURBITCOMPA(
    input [3:0] A,
    input [3:0] B,
    output [2:0] F
);
    wire [2:0]f1;
    wire [2:0]f2;
    reg [2:0]F;
    twobitcomp ros(A[3:2],B[3:2],f1);
    twobitcomp roshn(A[1:0],B[1:0],f2);
    always@(f1 or f2)
    begin
        if(f1==3'b100)
            F=3'b100;
        else
            F=f2;
        end
    endmodule
```

/\*\*F is concatenation of greater ,equal,less than quantities in the same order \*\*//



```
module top_decoder1(i0,i1,i2,en,o);
    input i0,i1,i2;
    input en;
    output [0:7]o;
    reg [0:7]o;
    always@(i0,i1,i2,en)
    begin
        if((en==1)&&(i0==0)&&(i1==0)&&(i2==0))
            o=8'b10000000;
        else if ((en==1)&&(i0==1)&&(i1==0)&&(i2==0))
            o=8'b01000000;
        else if ((en==1)&&(i0==0)&&(i1==1)&&(i2==0))
            o=8'b00100000;
        else if ((en==1)&&(i0==1)&&(i1==1)&&(i2==0))
            o=8'b00010000;
        else if ((en==1)&&(i0==0)&&(i1==0)&&(i2==1))
            o=8'b00001000;
        else if ((en==1)&&(i0==1)&&(i1==0)&&(i2==1))
            o=8'b00000100;
        else if ((en==1)&&(i0==0)&&(i1==1)&&(i2==1))
            o=8'b00000010;
        else if ((en==1)&&(i0==1)&&(i1==1)&&(i2==1))
            o=8'b00000001;
        else
            o=8'b00000000;
    end
endmodule
```





```
module top_decoder(i_bit,Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7);  
    input [2:0] i_bit;  
    output Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7;  
  
    assign Y0 = (~i_bit[2])&(~i_bit[1])&(~i_bit[0]);  
  
    assign Y1 = (~i_bit[2])&(~i_bit[1])&(i_bit[0]);  
  
    assign Y2 = (~i_bit[2])&(i_bit[1])&(~i_bit[0]);  
  
    assign Y3 = (~i_bit[2])&(i_bit[1])&(i_bit[0]);  
  
    assign Y4 = (i_bit[2])&(~i_bit[1])&(~i_bit[0]);  
  
    assign Y5 = (i_bit[2])&(~i_bit[1])&(i_bit[0]);  
  
    assign Y6 = (i_bit[2])&(i_bit[1])&(~i_bit[0]);  
  
    assign Y7 = (i_bit[2])&(i_bit[1])&(i_bit[0]);  
  
endmodule
```



# Outline

---

- Introductions
- **Verilog Syntax**
- Structural Modelling
- Behavioural Modelling
- State Machine
- Random but Important Stuff



---

# Verilog Syntax



# Module

---

**module** module\_name(port\_list);

Declarations:

Port declaration (input, output, inout,...)

Data type declaration (reg, wire , parameter,...)

Task and function declaration

Statements:

Initial block

**Behavioral**

Always block

Module instantiation

**Structural**

Gate Instantiation

UDP Instantiation

**Data-Flow**

Continuous assignment

**endmodule**



```
module FA_MIX (A, B, CIN, SUM, COUT);  
  input A,B,CIN;  
  output SUM, COUT;  
  reg COUT;  
  reg T1, T2, T3;  
  wire S1;  
  
  xor X1 (S1, A, B); // Gate instantiation.  
  
  always @ (A or B or CIN) // Always Block  
  begin  
    T1 = A & CIN;  
    T2 = B & CIN;  
    T3 = A & B;  
    COUT = (T1 | T2 | T3);  
  END  
  assign SUM = S1 ^ CIN; // Continuous assignment  
endmodule
```



# Lexical Conventions

---

- Case Sensitivity
  - Verilog HDL is case sensitive
- White Spaces
  - Blank Spaces, Tabs, New Line etc
- Comments
  - Single Line     //
  - Multiline       /\* Text   \*/
- Identifiers
  - Must begin with (**a-z, A-Z, \_**)
  - May Contain (**a-z, A-Z, \_, 0-9,\$**)
  - Upto **1024** character long



# Lexical Conventions

- [illegible]



# Lexical Conventions

---

- Ports
  - Input
  - Output
  - Inout
- Data Types
  - Nets - represent structural connections between components.
  - Registers - represent variables used to store data.





# Wire

Net Data Type	Functionality
wire, tri	Interconnecting wire - no special resolution function
wor, trior	Wired outputs OR together (models ECL)
wand, triand	Wired outputs AND together (models open-collector)
tri0, tri1	Net pulls-down or pulls-up when not driven
supply0, supply1	Net has a constant logic 0 or logic 1 (supply strength)
triereg	Retains last value, when driven by z (tristate).



# Reg

---

Data Type	Functionality
reg	Unsigned variable
integer	Signed variable - 32 bits
time	Unsigned integer - 64 bits
real	Double precision floating point variable



# Logic Values

---

Logic Value	Description
0	Zero, low, false
1	One, high, value
Z	High impedance, floating
X	Unknown, uninitialised



# Operators

- Arithmetic Operators  
`+, -, *, /`
- Relational Operators  
`>, <, <=, >=`
- Equality Operators  
`==, !=, ==, !=`
- Logical Operators  
`!, &&, ||`
- Bit-wise Operators  
`~, &, |, ^, ^~ or ~^`
- Reduction Operators  
`&, ~&, |, ~|, ^, ^~ or ~^`
- Shift Operators  
`<<, >>`
- Concatenation Operators  
`{a, b[3:0], c, 4'b1001}`
- Replication Operations  
`{n{m}}`
- Conditional Operations  
`cond_expr? true_expr: false_expr`



# Outline

---

- Introductions
- Verilog Syntax
- **Structural Modelling**
- Behavioural Modelling
- State Machine
- Random but Important Stuff



---

# Structural Modelling



# Structural Modelling

---

- When Verilog was first developed (1984) most logic simulators operated on netlists
- Netlist: list of gates and how they're connected
- A natural representation of a digital logic circuit
- Not the most convenient way to express test benches



# Module Instantiation

---

- Instances of
  - `module mymod(y, a, b);`
- look like
  - `mymod mm1(y1, a1, b1);` // Connect-by-position
  - `mymod (y2, a1, b1), (y3, a2, b2);` // Instance names omitted
  - `mymod mm2(.a(a2), .b(b2), .y(c2));` // Connect-by-name





# Gate Level Primitives

---

Verilog provides the following:

and	nand	logical AND/NAND
or	nor	logical OR/NOR
xor	xnor	logical XOR/XNOR
buf	not	buffer/inverter
bufif0	notif0	Tristate with low enable
bifif1	notif1	Tristate with high enable



# Delays on Primitive Instances

---

- Instances of primitives may include delays
  - `buf`                `b1(a, b);`        `// Zero delay`
  - `buf #3`            `b2(c, d);`        `// Delay of 3`
  - `buf #(4,5)`       `b3(e, f);`        `// Rise=4, fall=5`



# Outline

---

- Introductions
- Verilog Syntax
- Structural Modelling
- **Behavioural Modelling**
- State Machine
- Random but Important Stuff



---

# Behavioural Modelling



# Behavioral Modeling

---

- A much easier way to write testbenches
- Also good for more abstract models of circuits
  - Easier to write
  - Simulates faster
- More flexible
- Provides sequencing
- Verilog succeeded in part because it allowed both the model and the testbench to be described together



# Procedural Blocks

---

- initial : initial blocks execute only once at time zero (start execution at time zero).
- always : always blocks loop to execute over and over again; in other words, as the name suggests, it executes always.



# Blocking and Nonblocking assignment

---

- Blocking
  - $a=b$
  - Sequential
- Non-Blocking
  - $a \leq b$
  - Parallel



# The Conditional Statement

---

- If
- If-else
- If, elseif, ... , else





# The Case statement

---

```
case ()  
< case1 > : < statement >  
< case2 > : < statement >  
.....  
default : < statement >  
endcase
```

- casez : Treats z as don't care.
- casex : Treats x and z as don't care.

```
always @ (a or b or c or d or sel)  
case (sel)  
  0 : y = a;  
  1 : y = b;  
  2 : y = c;  
  3 : y = d;  
endcase
```



# Looping Statements

---

- Forever
  - The forever loop executes continually, the loop never ends
- Repeat
  - The repeat loop executes `< statement >` a fixed `< number >` of times.
- While
  - `while (< expression >) < statement >`
- For
  - `for (< initial assignment >; < expression >, < step assignment >) < statement >`



# Clock Generation

---

- initial begin  
    clk = 0;  
    forever begin  
        #10 clk = ~clk;  
    end
- Initial clk = 0;  
    always #10 clk = ~clk;



# Testbenches

```
module circuit_with_delay (A,B,C,x,y);  
input A,B,C;  
output x,y;  
wire e;  
and #(30) g1(e,A,B);  
or #(20) g3(x,e,y);  
not #(10) g2(y,C);  
endmodule
```

- ° **Module circuit\_with\_delay is instantiated**
- ° **reg keyword indicates that values are stored (driven)**
- ° **Stimulus signals are applied sequentially**
- ° **\$finish indicates simulation should end**

```
//Stimulus for simple circuit  
module stimcrct;  
reg A,B,C;  
wire x,y;  
circuit_with_delay cwd(A,B,C,x,y);  
initial  
begin  
A = 1'b0; B = 1'b0; C = 1'b0;  
#100  
A = 1'b1; B = 1'b1; C = 1'b1;  
#100 $finish;  
end  
endmodule
```



# Testbenches

---

```
module test;  
reg a, b, sel;
```

```
mux m(y, a, b, sel);
```

```
initial begin
```

```
    $monitor($time,, "a = %b b=%b sel=%b y=%b",  
              a, b, sel, y);
```

```
    a = 0; b = 0; sel = 0;
```

```
    #10 a = 1;
```

```
    #10 sel = 1;
```

```
    #10 b = 1;
```

```
end
```



# Outline

---

- Introductions
- Verilog Syntax
- Structural Modelling
- Behavioural Modelling
- **State Machine**
- Random but Important Stuff



---

# State Machine



# Modeling FSMs Behaviorally

---

- There are many ways to do it:
- Define the next-state logic combinationaly and define the state-holding latches explicitly
- Define the behavior in a single always @(posedge clk) block





# FSM with Combinational Logic

---

```
module FSM(o, a, b, reset);  
  output o;  
  reg o;  
  input a, b, reset;  
  reg [1:0] state, nextState;  
  
  always @(a or b or state)  
  case (state)  
    2'b00: begin  
      nextState = a ? 2'b00 : 2'b01;  
      o = a & b;  
    end  
    2'b01: begin nextState = 2'b10; o = 0; end  
  endcase
```



# FSM with Combinational Logic

```
always @(a or b or state)
case (state)
  2'b00: begin
    nextState = a ? 2'b00 : 2'b01;
    o = a & b;
  end
  2'b01: begin nextState = 2'b10; o = 0; end
endcase
```

This is a Mealy machine  
because the output is directly  
affected by any change on the  
input

```
always @(posedge clk or reset)
if (reset)
  state <= 2'b00;
else
  state <= nextState;
```



# FSM from a Single Always Block

```
module FSM(o, a, b);  
  output o; reg o;  
  input a, b;  
  reg [1:0] state;  
  
  always @(posedge clk or reset)  
    if (reset) state <= 2'b00;  
    else case (state)  
      2'b00: begin  
        state <= a ? 2'b00 : 2'b01;  
        o <= a & b;  
      end  
      2'b01: begin state <= 2'b10; o <= 0; end  
    endcase
```

Expresses Moore machine  
behavior:  
Outputs are latched  
Inputs only sampled at clock  
edges

Nonblocking assignments used  
throughout to ensure coherency.  
RHS refers to values calculated in  
previous clock cycle



# Outline

---

- Introductions
- Verilog Syntax
- Structural Modelling
- Behavioural Modelling
- State Machine
- **Random but Important Stuff**



---

# Random but Important Stuff



# Tools

---

- Icarus
  - Icarus Verilog is a free compiler implementation for the IEEE-1364 Verilog hardware description language.
- VCS
  - The Synopsys VCS® functional verification solution is the primary verification tool.
- Questasim
  - The Questa Advanced Simulator is the core simulation and debug engine of the Questa Verification Solution
- ModelSim
  - ModelSim packs an unprecedented level of verification capabilities in a cost-effective HDL simulation solution



# Tools

---

- ISE
  - Xilinx ISE (Integrated Synthesis Environment)[3] is a software tool produced by Xilinx for synthesis and analysis of HDL designs, enabling the developer to synthesize ("compile") their designs, perform timing analysis, examine RTL diagrams, simulate a design's reaction to different stimuli, and configure the target device with the programmer.
- Vivado
  - Vivado Design Suite is a software suite produced by Xilinx for synthesis and analysis of HDL designs, superseding Xilinx ISE with additional features for system on a chip development and high-level synthesis

Source: Wikipedia



# Tools

---

- Design Compiler
  - Synthesize a block-level RTL design to generate a gate-level netlist with acceptable post-placement timing and congestion
- Innovus
  - Embedded Processor: placement, optimization, routing, and clocking
- Spectre
  - Circuit Simulator provides fast, accurate SPICE-level simulation
- Virtuoso
  - Virtuoso Schematic Editor XL
  - Virtuoso Layout Suite XL
- Liberate
  - Cadence® Virtuoso® Liberate™ characterization solution is a cloud-ready, ultra-fast standard cell, I/O, and complex multi-bit-cell library characterization solution.





# Verilog Code - Where we can see

---

- DC netlist
- Cadence



# What we should not do?

---

- Forgetting else statement after if block
  - Generate Latches
- Updating the same variable in multiple always block
  - Critical Warning - Multiconnected net
- For loop depending on N
  - Hardware can't be dynamic



# What we can't do?

---

- Instantiate structural block inside behavioural code
  - Generate can be used to do that
- Always block with both sensitivity
  - Should be either edge sensitive or level sensitive



# Good Habits

---

- Always Comment your code
- Provide proper indentation
- Break your code in multiple modules or atleast multiple always block
- **Follow Honour code - Compulsory**



---

# FPGA



# Outline

---

- **Introductions**
- Logic Blocks
- Routing
- Demo on Basys3



# Introduction

---

- **FPGA - Field Programmable Gate Array**
- **FPGA - 1984**
  - Alternative to Programmable Logic Devices
- **Field Programmable Gate Array**
  - Two dimensional array of logic blocks and flip-flops
  - Electrically Programmable Switches for interconnections between logic blocks.
- **ASIC**
  - Custom IC : Fabrication Technology



# Introduction

---

- ASIC
  - High Performance
  - Low Power
  - Low Cost in high volumes
- FPGA
  - Low Development Cost
  - Short Time to Market
  - Reprogrammable





# Introduction

---

- Manufacturing cycle for ASIC is very costly, lengthy and engages lots of manpower
- Mistakes not detected at design time have large impact on development time and cost
- FPGAs are perfect for rapid prototyping of digital circuits
- Easy upgrades like in case of software
- Unique applications reconfigurable computing




# Logic Blocks

---


- Logic block
  - A configurable Hardware
  - Transistor to Microprocessors
- Logic blocks of an FPGA can be implemented by any of the following:
  - Transistor pairs
  - combinational gates like basic NAND gates or XOR gates
  - **n-input Lookup tables**
  - Multiplexers

# Logic Blocks

 

Source: [http://www.ee.columbia.edu/~kinget/EE6350\\_S16/04\\_FPGA\\_Tom\\_Robert\\_Harrison\\_Guanshun/architecture.html](http://www.ee.columbia.edu/~kinget/EE6350_S16/04_FPGA_Tom_Robert_Harrison_Guanshun/architecture.html)

# Logic Blocks

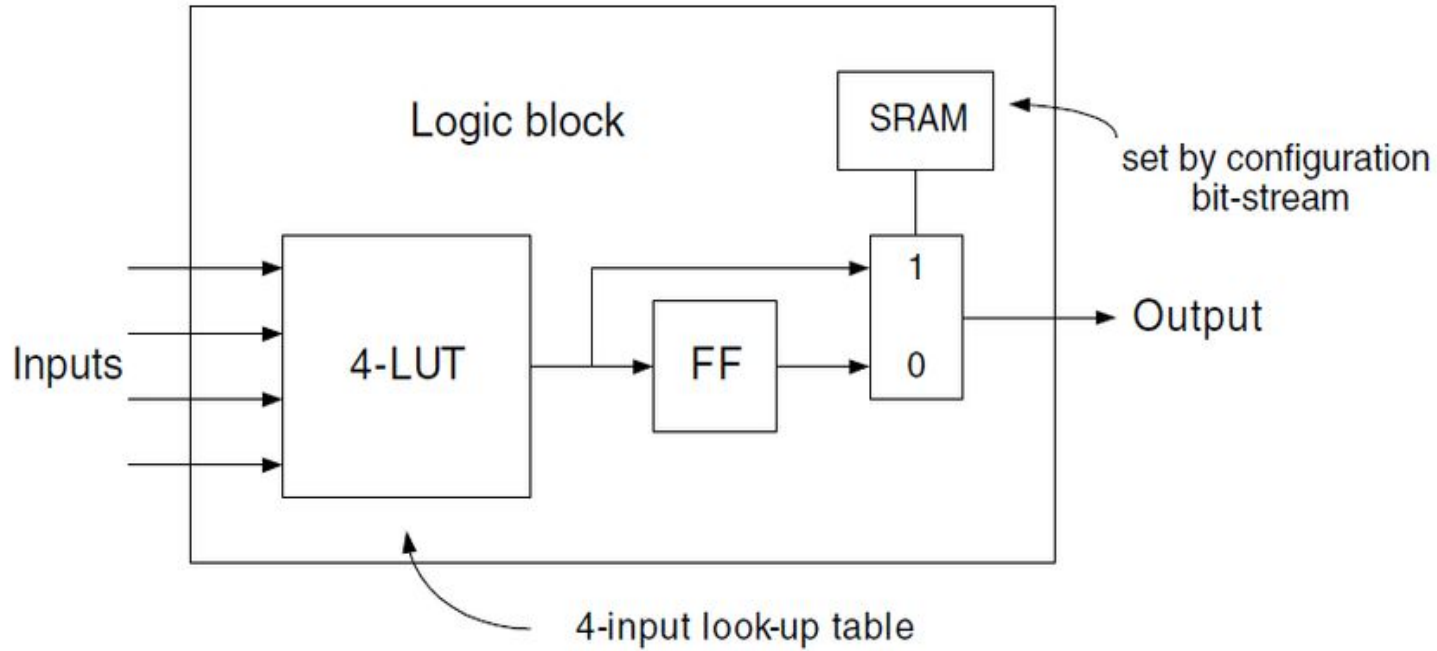

Source: [https://www.researchgate.net/figure/Figure-2-2-Basic-FPGA-configurable-logic-block-CLB\\_fig2\\_265553148](https://www.researchgate.net/figure/Figure-2-2-Basic-FPGA-configurable-logic-block-CLB_fig2_265553148)



# Routing

---

- Wire segments of varying lengths can be interconnected via electrically programmable switches.
- Density of logic block used in an FPGA depends on length and number of wire segments used for routing.
- Number of segments used for interconnection typically is a tradeoff between density of logic blocks used and amount of area used up for routing.



# Demo On Basys3

---

- <https://reference.digilentinc.com/reference/programmable-logic/basys-3/reference-manual>
- <https://reference.digilentinc.com/learn/programmable-logic/tutorials/basys-3-getting-started/start>



# Reference

---

- [http://www.asic-world.com/verilog/verilog\\_one\\_day2.html#Control\\_Statements](http://www.asic-world.com/verilog/verilog_one_day2.html#Control_Statements)
- [https://www.tutorialspoint.com/vlsi\\_design/vlsi\\_design\\_verilog\\_introduction.htm](https://www.tutorialspoint.com/vlsi_design/vlsi_design_verilog_introduction.htm)
- [http://www.referencedesigner.com/tutorials/verilog/verilog\\_01.php](http://www.referencedesigner.com/tutorials/verilog/verilog_01.php)
- <https://www.nandland.com/verilog/tutorials/tutorial-introduction-to-verilog-for-beginners.html>
- <http://vol.verilog.com/VOL/main.htm>
- <https://www.chipverify.com/verilog/verilog-design-abstraction-layers>
- [https://ece.umd.edu/courses/enee359a/verilog\\_tutorial.pdf](https://ece.umd.edu/courses/enee359a/verilog_tutorial.pdf)
- [web.cecs.pdx.edu/~mperkows/CLASS\\_VHDL\\_99/verilog.ppt](http://web.cecs.pdx.edu/~mperkows/CLASS_VHDL_99/verilog.ppt)
- <https://numato.com/kb/learning-fpga-verilog-beginners-guide-part-1-introduction/>



# Thank You

---